



A-LEVEL

Physics

7408/3BE

PAPER 3 SECTION B – Electronics

Mark scheme

June 2017

Version: 1.0 Final

Mark schemes are prepared by the Lead Assessment Writer and considered, together with the relevant questions, by a panel of subject teachers. This mark scheme includes any amendments made at the standardisation events which all associates participate in and is the scheme which was used by them in this examination. The standardisation process ensures that the mark scheme covers the students' responses to questions and that every associate understands and applies it in the same correct way. As preparation for standardisation each associate analyses a number of students' scripts. Alternative answers not already covered by the mark scheme are discussed and legislated for. If, after the standardisation process, associates encounter unusual answers which have not been raised they are required to refer these to the Lead Assessment Writer.

It must be stressed that a mark scheme is a working document, in many cases further developed and expanded on the basis of students' reactions to a particular paper. Assumptions about future mark schemes on the basis of one year's document should be avoided; whilst the guiding principles of assessment remain constant, details will change, depending on the content of a particular examination paper.

Further copies of this mark scheme are available from aqa.org.uk

Physics – Mark scheme instructions to examiners

1. General

The mark scheme for each question shows:

- the marks available for each part of the question
- the total marks available for the question
- the typical answer or answers which are expected
- extra information to help the Examiner make his or her judgement and help to delineate what is acceptable or not worthy of credit or, in discursive answers, to give an overview of the area in which a mark or marks may be awarded.

The extra information is aligned to the appropriate answer in the left-hand part of the mark scheme and should only be applied to that item in the mark scheme.

At the beginning of a part of a question a reminder may be given, for example: where consequential marking needs to be considered in a calculation; or the answer may be on the diagram or at a different place on the script.

In general the right-hand side of the mark scheme is there to provide those extra details which confuse the main part of the mark scheme yet may be helpful in ensuring that marking is straightforward and consistent.

2. Emboldening

- 2.1** In a list of acceptable answers where more than one mark is available ‘any **two** from’ is used, with the number of marks emboldened. Each of the following bullet points is a potential mark.
- 2.2** A bold **and** is used to indicate that both parts of the answer are required to award the mark.
- 2.3** Alternative answers acceptable for a mark are indicated by the use of **or**. Different terms in the mark scheme are shown by a / ; eg allow smooth / free movement.

3. Marking points

3.1 Marking of lists

This applies to questions requiring a set number of responses, but for which candidates have provided extra responses. The general principle to be followed in such a situation is that ‘right + wrong = wrong’.

Each error / contradiction negates each correct response. So, if the number of errors / contradictions equals or exceeds the number of marks available for the question, no marks can be awarded.

However, responses considered to be neutral (often prefaced by ‘Ignore’ in the mark scheme) are not penalised.

3.2 Marking procedure for calculations

Full marks can usually be given for a correct numerical answer without working shown unless the question states ‘Show your working’. However, if a correct numerical answer can be evaluated from incorrect physics then working will be required. The mark scheme will indicate both this and the credit (if any) that can be allowed for the incorrect approach.

However, if the answer is incorrect, mark(s) can usually be gained by correct substitution / working and this is shown in the ‘extra information’ column or by each stage of a longer calculation.

A calculation must be followed through to answer in decimal form. An answer in surd form is never acceptable for the final (evaluation) mark in a calculation and will therefore generally be denied one mark.

3.3 Interpretation of ‘it’

Answers using the word ‘it’ should be given credit only if it is clear that the ‘it’ refers to the correct subject.

3.4 Errors carried forward, consequential marking and arithmetic errors

Allowances for errors carried forward are likely to be restricted to calculation questions and should be shown by the abbreviation ECF or *conseq* in the marking scheme.

An arithmetic error should be penalised for one mark only unless otherwise amplified in the marking scheme. Arithmetic errors may arise from a slip in a calculation or from an incorrect transfer of a numerical value from data given in a question.

3.5 Phonetic spelling

The phonetic spelling of correct scientific terminology should be credited (eg fizix) **unless** there is a possible confusion (eg defraction/refraction) with another technical term.

3.6 Brackets

(.....) are used to indicate information which is not essential for the mark to be awarded but is included to help the examiner identify the sense of the answer required.

3.7 Ignore / Insufficient / Do not allow

‘Ignore’ or ‘insufficient’ is used when the information given is irrelevant to the question or not enough to gain the marking point. Any further correct amplification could gain the marking point.

‘Do **not** allow’ means that this is a wrong answer which, even if the correct answer is given, will still mean that the mark is not awarded.

3.8 Significant figure penalties

Answers to questions in the practical sections (7407/2 – Section A and 7408/3A) should display an appropriate number of significant figures. For non-practical sections, an A-level paper may contain up to 2 marks (1 mark for AS) that are contingent on the candidate quoting the **final** answer in a calculation to a specified number of significant figures (sf). This will generally be assessed to be the number of sf of the datum with the least number of sf from which the answer is determined. The mark scheme will give the range of sf that are acceptable but this will normally be the sf of the datum (or this sf -1).

An answer in surd form cannot gain the sf mark. An incorrect calculation **following some working** can gain the sf mark. For a question beginning with the command word ‘Show that...’, the answer should be

quoted to **one more** sf than the sf quoted in the question eg ‘Show that X is equal to about 2.1 cm’ – answer should be quoted to 3 sf. An answer to 1 sf will not normally be acceptable, unless the answer is an integer eg a number of objects. In non-practical sections, the need for a consideration will be indicated in the question by the use of ‘Give your answer to an appropriate number of significant figures’.

3.9 Unit penalties

An A-level paper may contain up to 2 marks (1 mark for AS) that are contingent on the candidate quoting the correct unit for the answer to a calculation. The need for a unit to be quoted will be indicated in the question by the use of ‘State an appropriate SI unit for your answer’. Unit answers will be expected to appear in the most commonly agreed form for the calculation concerned; strings of fundamental (base) units would not. For example, 1 tesla and 1 weber/metre² would both be acceptable units for magnetic flux density but 1 kg m² s⁻² A⁻¹ would not.

3.10 Level of response marking instructions

Level of response mark schemes are broken down into three levels, each of which has a descriptor. The descriptor for the level shows the average performance for the level. There are two marks in each level.

Before you apply the mark scheme to a student’s answer read through the answer and annotate it (as instructed) to show the qualities that are being looked for. You can then apply the mark scheme.

Determining a level

Start at the lowest level of the mark scheme and use it as a ladder to see whether the answer meets the descriptor for that level. The descriptor for the level indicates the different qualities that might be seen in the student’s answer for that level. If it meets the lowest level then go to the next one and decide if it meets this level, and so on, until you have a match between the level descriptor and the answer. With practice and familiarity you will find that for better answers you will be able to quickly skip through the lower levels of the mark scheme.


When assigning a level you should look at the overall quality of the answer and not look to pick holes in small and specific parts of the answer where the student has not performed quite as well as the rest. If the answer covers different aspects of different levels of the mark scheme you should use a best fit approach for defining the level and then use the variability of the response to help decide the mark within the level. i.e. if the response is predominantly level 2 with a small amount of level 3 material it would be placed in level 2.

The exemplar materials used during standardisation will help you to determine the appropriate level. There will be an answer in the standardising materials which will correspond with each level of the mark scheme. This answer will have been awarded a mark by the Lead Examiner. You can compare the student’s answer with the example to determine if it is the same standard, better or worse than the example. You can then use this to allocate a mark for the answer based on the Lead Examiner’s mark on the example.

You may well need to read back through the answer as you apply the mark scheme to clarify points and assure yourself that the level and the mark are appropriate.


Indicative content in the mark scheme is provided as a guide for examiners. It is not intended to be exhaustive and you must credit other valid points. Students do not have to cover all of the points mentioned in the indicative content to reach the highest level of the mark scheme

An answer which contains nothing of relevance to the question must be awarded no marks.

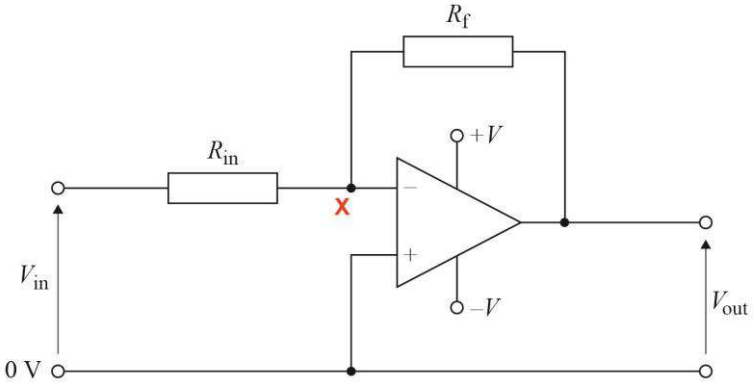
Question	Answers	Additional Comments/Guidelines	Mark
01.1		Correct position of X:	1
01.2	The non-inverting input	(non-inverting):	1
01.3	$I = (V_{in} - V_x) / R_{in} = (V_x - V_{out}) / R_f$ But $V_x = 0 \text{ V}$ (a virtual earth) $I = V_{in} / R_{in} = -V_{out} / R_f$ $\frac{V_{out}}{V_{in}} = -\frac{R_f}{R_{in}}$	Making use of: $I_{in} = -I_f$ Making use of virtual earth concept:	1 1
01.4	Voltage gain (Channel 1) = $-\frac{R_f}{R_{in1}}$ $-(150 \text{ k}\Omega / 7.5 \text{ k}\Omega)$ -20	Both number and sign must be correct:	1
01.5	$V_{out} = -R_f (V_{in \text{ Ch1}} / R_1 + V_{in \text{ Ch2}} / R_2)$ $= -150 \text{ k}\Omega ((15 \text{ mV} / 7.5 \text{ k}\Omega) + (-100 \text{ mV} / 30 \text{ k}\Omega))$ $= -((0.3) + (-0.5)) = 0.2 \text{ Volts}$	Evidence of correct method: Answer and correct sign:	1 1

Question	Answers	Additional Comments/Guidelines	Mark
01.6	By using variable resistors: The gain can easily be changed or the relative levels of the two channels can be set or the required balance between the two signals can be made	One relevant point made:	1
Total			8

Question	Answers	Additional Comments/Guidelines	Mark																																																																																																			
02.1	<table border="1"> <thead> <tr> <th data-bbox="322 309 465 411">Number shown on die</th> <th colspan="3" data-bbox="465 309 687 411">Logic inputs</th> <th colspan="7" data-bbox="687 309 1339 411">Logic outputs</th> </tr> <tr> <th data-bbox="322 411 465 448"></th> <th data-bbox="465 411 528 448">C</th> <th data-bbox="528 411 607 448">B</th> <th data-bbox="607 411 687 448">A</th> <th data-bbox="687 411 766 448">L1</th> <th data-bbox="766 411 837 448">L2</th> <th data-bbox="837 411 927 448">L3</th> <th data-bbox="927 411 1016 448">L4</th> <th data-bbox="1016 411 1106 448">L5</th> <th data-bbox="1106 411 1196 448">L6</th> <th data-bbox="1196 411 1339 448">L7</th> </tr> </thead> <tbody> <tr> <td data-bbox="322 448 465 496">1</td> <td data-bbox="465 448 528 496">0</td> <td data-bbox="528 448 607 496">0</td> <td data-bbox="607 448 687 496">0</td> <td data-bbox="687 448 766 496">0</td> <td data-bbox="766 448 837 496">0</td> <td data-bbox="837 448 927 496">0</td> <td data-bbox="927 448 1016 496">0</td> <td data-bbox="1016 448 1106 496">0</td> <td data-bbox="1106 448 1196 496">0</td> <td data-bbox="1196 448 1339 496">1</td> </tr> <tr> <td data-bbox="322 496 465 544">2</td> <td data-bbox="465 496 528 544">0</td> <td data-bbox="528 496 607 544">0</td> <td data-bbox="607 496 687 544">1</td> <td data-bbox="687 496 766 544">1</td> <td data-bbox="766 496 837 544">0</td> <td data-bbox="837 496 927 544">0</td> <td data-bbox="927 496 1016 544">0</td> <td data-bbox="1016 496 1106 544">0</td> <td data-bbox="1106 496 1196 544">1</td> <td data-bbox="1196 496 1339 544">0</td> </tr> <tr> <td data-bbox="322 544 465 592">3</td> <td data-bbox="465 544 528 592">0</td> <td data-bbox="528 544 607 592">1</td> <td data-bbox="607 544 687 592">0</td> <td data-bbox="687 544 766 592">1</td> <td data-bbox="766 544 837 592">0</td> <td data-bbox="837 544 927 592">0</td> <td data-bbox="927 544 1016 592">0</td> <td data-bbox="1016 544 1106 592">0</td> <td data-bbox="1106 544 1196 592">1</td> <td data-bbox="1196 544 1339 592">1</td> </tr> <tr> <td data-bbox="322 592 465 639">4</td> <td data-bbox="465 592 528 639">0</td> <td data-bbox="528 592 607 639">1</td> <td data-bbox="607 592 687 639">1</td> <td data-bbox="687 592 766 639">1</td> <td data-bbox="766 592 837 639">0</td> <td data-bbox="837 592 927 639">1</td> <td data-bbox="927 592 1016 639">1</td> <td data-bbox="1016 592 1106 639">0</td> <td data-bbox="1106 592 1196 639">1</td> <td data-bbox="1196 592 1339 639">0</td> </tr> <tr> <td data-bbox="322 639 465 687">5</td> <td data-bbox="465 639 528 687">1</td> <td data-bbox="528 639 607 687">0</td> <td data-bbox="607 639 687 687">0</td> <td data-bbox="687 639 766 687">1</td> <td data-bbox="766 639 837 687">0</td> <td data-bbox="837 639 927 687">1</td> <td data-bbox="927 639 1016 687">1</td> <td data-bbox="1016 639 1106 687">0</td> <td data-bbox="1106 639 1196 687">1</td> <td data-bbox="1196 639 1339 687">1</td> </tr> <tr> <td data-bbox="322 687 465 735">6</td> <td data-bbox="465 687 528 735">1</td> <td data-bbox="528 687 607 735">0</td> <td data-bbox="607 687 687 735">1</td> <td data-bbox="687 687 766 735">1</td> <td data-bbox="766 687 837 735">1</td> <td data-bbox="837 687 927 735">1</td> <td data-bbox="927 687 1016 735">1</td> <td data-bbox="1016 687 1106 735">1</td> <td data-bbox="1106 687 1196 735">1</td> <td data-bbox="1196 687 1339 735">0</td> </tr> <tr> <td data-bbox="322 735 465 815">Reset 6 → 1</td> <td colspan="3" data-bbox="465 735 687 815"></td> <td data-bbox="687 735 766 815"></td> <td data-bbox="766 735 837 815"></td> <td data-bbox="837 735 927 815"></td> <td data-bbox="927 735 1016 815"></td> <td data-bbox="1016 735 1106 815"></td> <td data-bbox="1106 735 1196 815"></td> <td data-bbox="1196 735 1339 815"></td> </tr> </tbody> </table>	Number shown on die	Logic inputs			Logic outputs								C	B	A	L1	L2	L3	L4	L5	L6	L7	1	0	0	0	0	0	0	0	0	0	1	2	0	0	1	1	0	0	0	0	1	0	3	0	1	0	1	0	0	0	0	1	1	4	0	1	1	1	0	1	1	0	1	0	5	1	0	0	1	0	1	1	0	1	1	6	1	0	1	1	1	1	1	1	1	0	Reset 6 → 1											One mark for each full pattern of L1 and L6 :	2
Number shown on die	Logic inputs			Logic outputs																																																																																																		
	C	B	A	L1	L2	L3	L4	L5	L6	L7																																																																																												
1	0	0	0	0	0	0	0	0	0	1																																																																																												
2	0	0	1	1	0	0	0	0	1	0																																																																																												
3	0	1	0	1	0	0	0	0	1	1																																																																																												
4	0	1	1	1	0	1	1	0	1	0																																																																																												
5	1	0	0	1	0	1	1	0	1	1																																																																																												
6	1	0	1	1	1	1	1	1	1	0																																																																																												
Reset 6 → 1																																																																																																						
02.2	L7 = NOT A; Accept: $L7 = \bar{A}$	Delete previous comment	1																																																																																																			

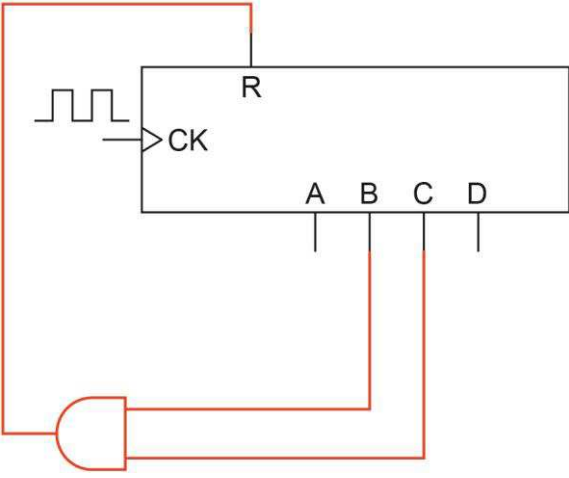Question	Answers	Additional Comments/Guidelines	Mark
02.3	 <p>The diagram shows a 4-bit register with inputs A, B, C, and D. A clock input CK is connected to a square wave pulse. A reset input R is connected to the output of a 2-input AND gate. The inputs of the AND gate are B and C. The output of the AND gate is connected to the R input of the register.</p>	<p>1 mark for reset condition from B and C: 1 mark for use of a single 2-input AND gate:</p> <p>(accept correct implementation of the full reset code $\bar{A}.B.C$ for 1 mark)</p>	2

Question	Answers	Additional Comments/Guidelines	Mark
02.4		<p>1 mark - NOT gate from B:</p> <p>1 mark - AND gate from \bar{B} and C:</p> <p>1 mark - OR gate connecting the two conditions:</p>	3
Total			8

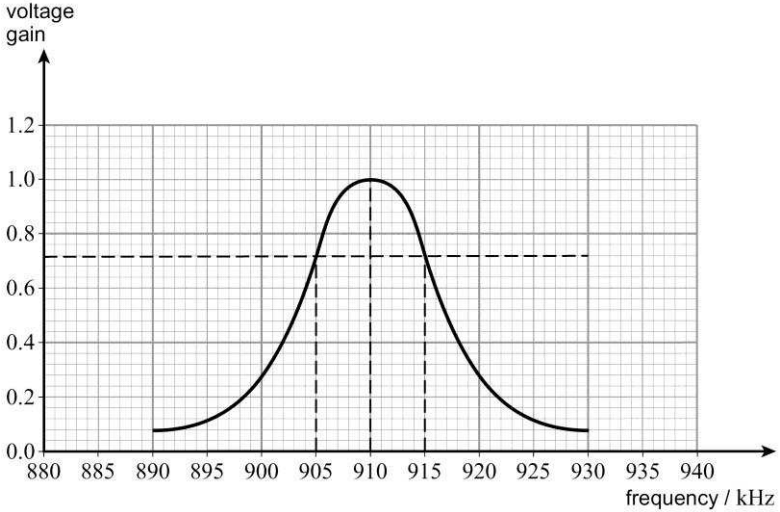Question	Answers	Additional Comments/Guidelines	Mark
03.1	$f = 1 / (2\pi \sqrt{LC})$ $C = 1 / f^2 4\pi^2 L$ $C = 1 / (910 \times 10^3)^2 \times 4 \times \pi^2 \times 1.1 \times 10^{-3}$ $C = 27.8 \text{ pF}$ (accept 28pF)	Formula with correct substitution / evidence of correct working: Answer:	1 1
03.2		General shape around f_0 and to max of 1.0 on relative voltage gain axis 10 kHz bandwidth at 0.71 gain Frequencies (905 – 910 – 915) kHz (identified / used)	1 1 1
03.3	Smaller Q factor leads to: (Any two from) (i) Broader bandwidth (ii) More noise / (hiss) detected (iii) Less selectivity (iv) More susceptible to crosstalk from neighbouring stations on the frequency spectrum. (v) Less gain due to energy loss / loss of signal detail		2

Total			7
--------------	--	--	----------

Question	Answers	Additional Comments/Guidelines	Mark										
04.1	Photoconductive (accept reverse bias)		1										
04.2	<table border="1" style="width: 100%; border-collapse: collapse;"> <tr> <td style="width: 80%;"></td> <td style="width: 20%; text-align: center;">Tick (✓) if correct</td> </tr> <tr> <td>Non-inverting amplifier</td> <td></td> </tr> <tr> <td>Comparator</td> <td style="text-align: center;">✓</td> </tr> <tr> <td>Summing amplifier</td> <td></td> </tr> <tr> <td>Difference amplifier</td> <td></td> </tr> </table>		Tick (✓) if correct	Non-inverting amplifier		Comparator	✓	Summing amplifier		Difference amplifier			1
	Tick (✓) if correct												
Non-inverting amplifier													
Comparator	✓												
Summing amplifier													
Difference amplifier													
04.3	Light level ~ 1000 lux +/- 10%		1										
04.4	$V_x = IR$; $V_x = 100 \mu A \times 20 k\Omega = 2 V$		1										
04.5	Rule that if $V_- > V_+$ then V_{out} is 0 V (low) Voltage drop across LED so LED is ON	Do not allow LED is ON if supported by incorrect reason	1 1										
Total			6										

Question	Answers	Additional Comments/Guidelines	Mark
05	<p>Expected information:</p> <p>Longwave f ~ 150 kHz - 300 kHz λ ~ 2 km – 1 km Aerial Very long Mode Ground (surface) wave – diffracted Application Some national radio – large coverage National time signal</p> <p>Shortwave f ~ 3 Mhz - 30 MHz λ ~ 100 m – 10 m Aerial medium Mode Sky wave – reflected from ionosphere (above ~ 500 kHz) Application Some national radio – large coverage Long distance comms. for ships and planes Amateur radio enthusiasts</p> <p>Microwave f ~ 100 GHz - 2 GHz λ ~ 3 mm – 150 mm Aerial Very short Mode Direct (space) wave -terrestrial line of sight hops OR space satellite Application 3G telephone network</p>	<p>1–2 marks: A limited answer with significant detail missing. Candidates may be able to recall terms such as ‘sky waves’ & ‘ground waves’, but there may be confusion as to the spectral frequencies or application. The material may lack organisation and technical terms may not be fully understood or used incorrectly.</p> <p>3–4 marks: The roles of at least two links are covered and most of the detail is present. There will be some structure, but it may be either brief or unclear in parts.</p> <p>5–6 marks: All three links are covered in detail. The candidate shows good knowledge and uses technical terms correctly. The answer has structure and clearly conveys the information required by the question. The candidate may show a depth of understanding that goes beyond basic recall.</p>	6

	Satellite TV Data transfer to remote locations eg (Falkland Islands)		
Total			6